


Exercice 4:

Machine asynchrone

stator Δ

rotor 1
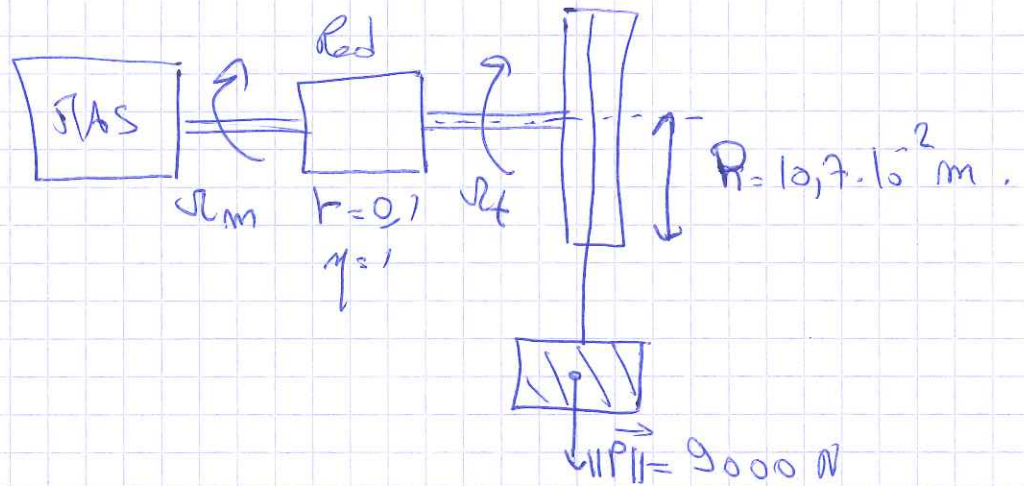
$$U_{\text{reseau}} = 220 \text{ V} \quad f = 50 \text{ Hz}$$



Essai à vide: $U_0 = 220 \text{ V}$ $I_0 = 10 \text{ A}$ $P_0 = 305 \text{ W}$

Essai en CC: $U_{cc} = 72,5 \text{ V}$ $I_{cc} = 30 \text{ A}$ $P_{cc} = 1400 \text{ W}$

rotor bloqué

1/ Vitesse de déplacement $v = 1 \text{ m} \cdot \text{s}^{-1}$

Ω_{rotor} !

$$\Omega_m = \frac{\Omega_t}{r} \text{ (en rad/s)}$$

$$\Omega_t = \frac{v}{R} = \frac{1}{10,7 \cdot 10^{-2}} = 9,34 \text{ rad} \cdot \text{s}^{-1}$$

$$\boxed{\Omega_m} = \frac{\Omega_t}{r} = \frac{9,34}{0,1} = \boxed{93,4 \text{ rad} \cdot \text{s}^{-1}}$$

$p = ?$ $m_m = \frac{\Omega}{2\pi} \times 60 = 891,9$

$p = 3$ donne $m_s = \frac{f \times 60}{3} = 1000 \text{ tr} \cdot \text{min}^{-1}$

g?

$$g = \frac{m_{ms} - m_{am}}{m_{ms}} = \frac{1000 - 891,9}{1000}$$

$$g = 0,109$$

P_U = ?

$$T_U = T_r \Rightarrow T_r = P_{bit} R$$
$$T_r = 9000 \times 6,7 \cdot 10^{-2}$$

$$T_U = T_r = 963 \text{ Nm}$$

Coefficient η reducteur = 0,1, on peut

écrite

$$P_{U_{\text{mot}}} = P_{U_{\text{treuil}}} = T_{U_{\text{rotateur}}} \times \Omega_{\text{rotateur}} = T_{U_{\text{treuil}}} \times \Omega_{\text{treuil}}$$

$$P_{U_{\text{rot}}} = T_{U_{\text{rot}}} \times \Omega_{\text{rot}}$$
$$(P_{U_{\text{rot}}} = T_{U_{\text{treuil}}} \times \Omega_{\text{treuil}}) \Rightarrow T_{U_{\text{rot}}} = T_{U_{\text{treuil}}} \times \frac{\Omega_{\text{treuil}}}{\Omega_{\text{rotateur}}}$$

$$= T_{U_{\text{treuil}}} \times i$$

$$T_{U_{\text{rot}}} = 963 \times 0,1 = 96,3 \text{ Nm}$$

$$P_{U_{\text{rot}}} = 963 \times 9,34 = 8994,4 \text{ W}$$


P_{abs} ?
I_{ligne} ?

$$P_{\text{abs}} = \frac{P_{U_{\text{rot}}}}{\eta_m} = \frac{8994,4}{0,84}$$

$$P_{\text{abs}} = 10707,61 \text{ W}$$


$$I_{\text{ligne}} = \frac{P_{\text{abs}}}{\sqrt{3} \cdot U_{\text{ca}} \cdot \eta} = \frac{10707,6}{\sqrt{3} \times 220 \times 0,83} = 33,85 \text{ A}$$

ex 4 (suite)

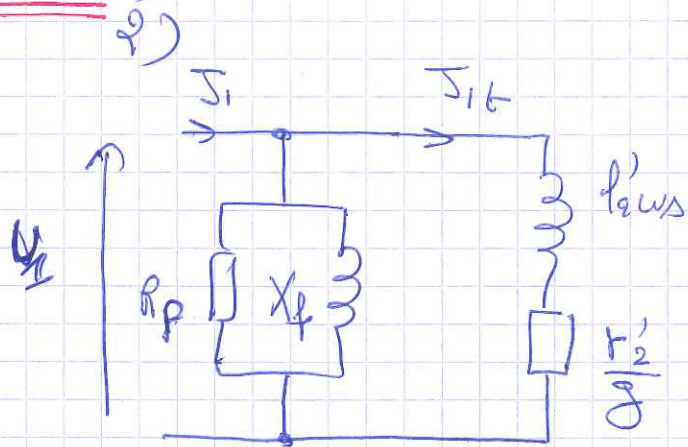

I_L est le courant polygonal et non par I_L le courant en ligne.

2.1)

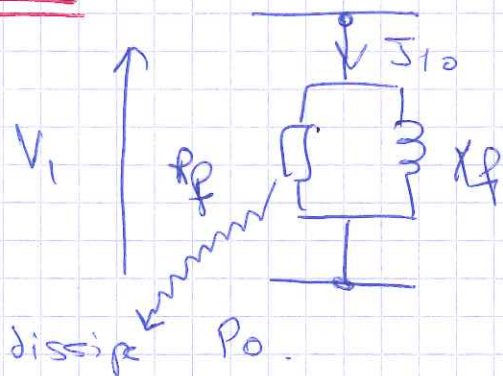

$$I_{10} = 10A$$

$$I_{L0} = \frac{I_{10}}{\sqrt{3}}$$

$$I_{L0} = \frac{10}{\sqrt{3}} = 5,77A$$

$$P_0 = 3 \times \frac{U_1^2}{R_f}$$

$$\Rightarrow R_f = \frac{3U_1^2}{P_0}$$

$$R_f = \frac{3 \times 220^2}{305}$$

$$R_f = 476,06 \Omega$$

$$Q_0 = 3 \frac{U_1^2}{X_f}$$

$$X_f = \frac{3U_1^2}{\sqrt{S_{10}^2 - P_0^2}}$$

$$S_{10} = \sqrt{3} U_1 I_{L0} = \sqrt{3} \times 220 \times 10$$

$$S_{10} = 3810,5 VA$$

$$X_f = \frac{3 \times 220^2}{\sqrt{3810,5^2 - 305^2}} = \frac{145200}{\sqrt{\quad}}$$

$$X_f = \frac{145200}{3798} = 38,22 \Omega$$

22.)

Essai en CC.

$$\begin{aligned} S_{cc} &= \sqrt{3} \times V_{cc} \times I_{cc} \\ &= \sqrt{3} \times 72,5 \times 30 \\ &= \sqrt{3} \times 2175 \end{aligned}$$

$$S_{cc} = 3767,2 \text{ VA}$$

$$P_{cc} = 1400 \text{ W}$$


$$Q_{cc} = \sqrt{S_{cc}^2 - P_{cc}^2} = \sqrt{3767,2^2 - 1400^2}$$

$$Q_{cc} = 3497,4 \text{ VAR}$$

$$P_{\text{rot}} = \frac{3U_1^2}{R_2}$$

$g = 1$ (à rotation bloquée)
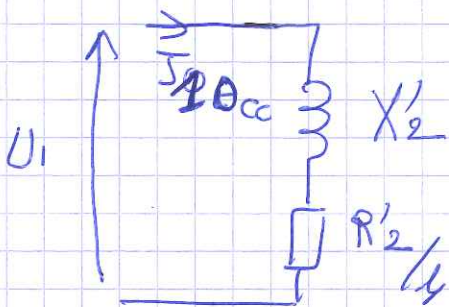
$$\cancel{P_{cc}} = \cancel{3R_2' I_{10cc}^2} + \cancel{3R_2' I_{10cc}^2}$$



$$P_{cc} = 3R_2' I_{10cc}^2$$

$$I_{10cc} = 30 \text{ A}$$

$$I_{10cc} = \frac{I_{cc}}{\sqrt{3}}$$

$$I_{10cc} = \frac{30}{\sqrt{3}} = 17,32 \text{ A}$$

$$R_2' = \frac{P_{cc}}{3 I_{10cc}^2}$$

$$R_2' = \frac{1400}{3 \times 17,32^2} = 1,55 \Omega$$

$$\cancel{Q_{cc}} = \cancel{3X_2' I_{10cc}^2}$$

$$Q_{cc} = 3X_2' I_{10cc}^2$$

$$X_2' = \frac{Q_{cc}}{3 I_{10cc}^2} = \frac{3497,4}{3 \times 17,32^2} = 3,78 \Omega$$

ex 4 (Suite)

3/

$$\underline{G} = \frac{1}{R_f} + \frac{1}{jX_f} + \frac{1}{\left(\frac{R'_2}{g} + jX'_2\right)}$$

$$= \frac{1}{R_f} + \frac{1}{jX_f} + \frac{\frac{R'_2}{g} - jX'_2}{\left(\frac{R'_2}{g}\right)^2 + X'^2_2}$$

$$= \frac{1}{R_f} + \frac{\frac{R'_2}{g}}{\left(\frac{R'_2}{g}\right)^2 + X'^2_2} + \frac{1}{jX_f} + \frac{1}{j} \left(- \frac{X'_2}{\left(\frac{R'_2}{g}\right)^2 + X'^2_2} \right)$$

$$\underline{G} = \frac{1}{R} + \frac{1}{jX}$$

donc

$$\left[\frac{1}{R} = \frac{1}{R_f} + \frac{\frac{R'_2}{g}}{\left(\frac{R'_2}{g}\right)^2 + X'^2_2} \right]$$

et

$$\left[\frac{1}{X} = \frac{1}{X_f} - \frac{X'_2}{\left(\frac{R'_2}{g}\right)^2 + X'^2_2} \right]$$

4/ Si: g petit-

$$\frac{1}{R} = \frac{1}{R_f} + \frac{\frac{R'_2}{g}}{\left(\frac{R'_2}{g}\right)^2}$$

$$= \frac{1}{R_f} + g \cdot \frac{1}{R'_2} = \frac{1}{476,06} + g \frac{1}{1,55}$$

$$\boxed{\frac{1}{R} = 2,1 \cdot 10^{-3} + g \cdot 0,64}$$

$$\frac{1}{X} = \frac{1}{X_f} - g^2 \cdot \frac{X'_2}{R'_2} = \frac{1}{38,22} + (-) g^2 \frac{3,88}{1,552}$$

$$\left[\frac{1}{X} = 0,0261 - g^2 \cdot 1,614 \right]$$

5) Im preind $\frac{1}{R} = 0,002 + 0,65 g$

$$\frac{1}{X} = 0,025 + 1,5 \cdot g^2$$

A.N.

$$\frac{1}{R} = 2 \cdot 10^{-3} + 0,11 \cdot 0,65$$

$$= 2 \cdot 10^{-3} + 71,5 \cdot 10^{-3}$$


$$= 73,5 \cdot 10^{-3}$$

$$\underline{\underline{R}} = \frac{1}{73,5 \cdot 10^{-3}} = \underline{\underline{13,6 \Omega}}$$

$$\frac{1}{X} = 0,025 + 1,5 \times 0,11^2$$

$$= 43,15 \cdot 10^{-3}$$
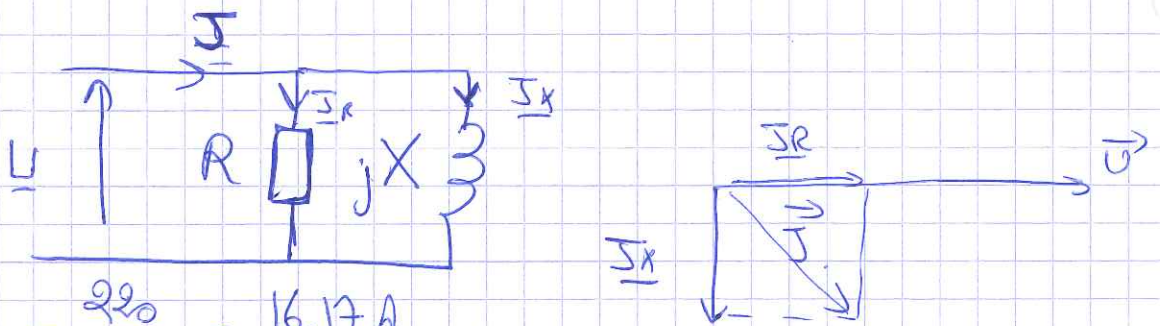
$$\underline{\underline{X}} = \frac{1}{43,15 \cdot 10^{-3}} = \underline{\underline{23,174 \Omega}}$$



$$I_R = \frac{U}{R} = \frac{220}{13,6} = 16,17 A$$

$$I_X = \frac{U}{X} = \frac{220}{23,17} = 9,49 A$$

$$I = \sqrt{(I_R)^2 + (I_X)^2}$$

$$I = \sqrt{3} \times I = \sqrt{3} \times \sqrt{16,17^2 + 9,49^2}$$

$$\underline{\underline{I}} = \sqrt{3} \times 18,74 = \underline{\underline{32,47 A}}$$