

Exercice 5.

Um motor síncrono $p=3$ (6 pólos)

stator em 1

rotor bobinado couple em 1

$$U_{\text{stator}} = 380 \text{ V} ; f = 50 \text{ Hz}$$

$$R_{\text{stat}} = 20 \cdot 10^{-3} \Omega$$

$$R_{\text{rot}} = 30 \cdot 10^{-3} \Omega$$

$$P_{\text{fer}} = 4800 \text{ W}$$

$$P_{\text{meca}} = 1300 \text{ W} \quad \text{a} \quad m_s \text{ nominal.} \quad \frac{1}{\text{de } m_s} \quad \text{C}^{\text{st}} \text{ outrem}$$

$$I_0 = 74 \text{ A. (a} \text{ vide)}$$

Essai em court circuit:

$$U_{cc} = 72 \text{ V.}$$

$$I_{cc} = 220 \text{ A.}$$

$$P_{cc} = 7200 \text{ W.}$$

1) Em regime nominal

$$\rightarrow P_{0n} = 116 \text{ kW} \quad \rightarrow g_m = 2,6 \%$$

$$\rightarrow S_N = 145 \text{ kVA.}$$

m?

$$g_m = \frac{m_s - m}{m_s}$$

$$p=3 \Rightarrow \underline{m_s} = \frac{60 \times f}{p} = \frac{60 \times 50}{3} = 1000 \text{ tr. min}^{-1}$$


$$g_m \cdot m_s = m_s - m$$

$$\underline{m = m_s (1 - g)}$$

$$m = 1000 \left(1 - \frac{2,6}{100}\right)$$
$$\underline{m = 974 \text{ tr. min}^{-1}}$$

Exe 5 (Suite)

1) Bilan de puissance :

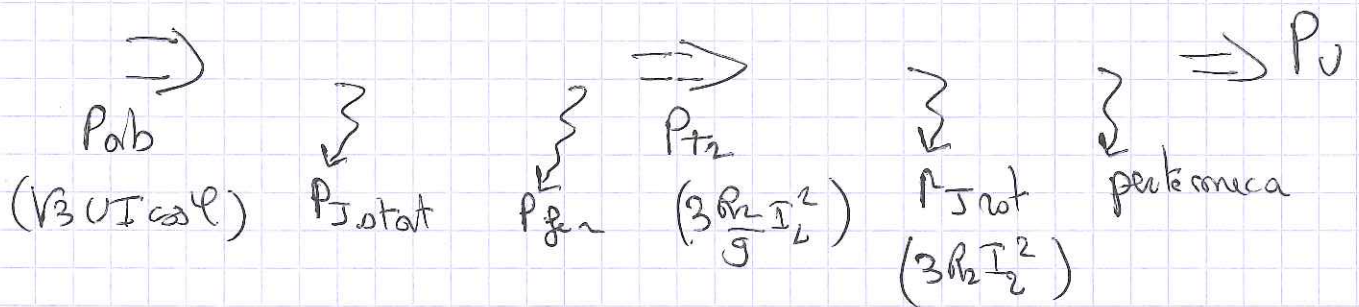

au point de fonctionnement nominal, on

a :

$$I_{\text{ligne}} = \frac{S_N}{\sqrt{3} \cdot U} = \frac{145 \cdot 10^3}{\sqrt{3} \cdot 380} = 220,3 \text{ A}$$

$$P_{J_{\text{total}}} = 3 R_1 I_{\text{ligne}}^2 = 3 \times 20 \cdot 10^{-3} \cdot (220,3)^2 = 2911,92 \text{ W}$$

$$\text{Pertes fer} = 4800 \text{ W}$$

P_{TR} ?

$$P_{tr} = \frac{3R_2}{g} I_2^2 \quad \text{et} \quad P_{J_{\text{rot}}} = 3R_2 I_2^2 = P_{tr} \cdot g$$

On peut écrire que :

$$P_{TR} = P_u + p_{\text{meca}} + P_{J_{\text{rot}}}$$
$$= P_u + p_{\text{meca}} + P_{TR} \cdot g$$

$$P_{TR} (1-g) = P_u + p_{\text{meca}}$$

$$P_{TR} = \frac{P_u + p_{\text{meca}}}{(1-g)} = \frac{116 \cdot 10^3 + 1300}{\left(1 - \frac{2,6}{100}\right)}$$

$$P_{TR} = 120,431 \text{ kW}$$

$$P_{\text{stator}} = 2911 \text{ W} \quad P_f = 4800 \text{ W}$$

$$\text{et } P_{\text{tr}} = 120431.$$

$$\begin{aligned} \text{d'où } P_{\text{abs}} &= P_{\text{tr}} + P_{\text{stator}} + P_f \\ &= 120431 + 2911 + 4800 \end{aligned}$$

$$P_{\text{abs}} = 128142 \text{ W}$$

$$\underline{\cos \varphi = ?}$$

$$\cos \varphi = \frac{P_{\text{abs}}}{S_{\text{abs}}} = \frac{128142}{145}$$

$$\cos \varphi = 0,8837$$

$$\underline{\eta = ?}$$

$$\eta = \frac{P_o}{P_a} = \frac{116}{128142} = 0,905$$

$$\underline{T_{\text{em}} ?}$$

$$T_{\text{em}} = \frac{P_{\text{tr}}}{\Omega} = \frac{120431}{\left(\frac{2\pi \times 1000}{60}\right)}$$

$$T_{\text{em}} = \frac{120431}{104,71} = 1150 \text{ Nm}$$

$$\underline{T_o ?}$$

$$T_o = \frac{P_o}{\Omega} = \frac{116 \cdot 10^3}{\left(\frac{2\pi \times 974}{60}\right)} = \frac{116 \cdot 10^3}{101,99}$$

$$T_o = 1137,28 \text{ Nm}$$

ex 5 (Suite)

2) Etablissement du modèle.

- Essai à vide R_f, X_f .

$$P_f = 4800 \text{ W} = 3 \cdot \frac{V^2}{R_f}$$

$$R_f = \frac{3 \cdot V^2}{4800} = \frac{3 \cdot 220^2}{4800}$$

$$R_f = 30,25 \Omega$$

À vide, on absorbe $I_0 = 74 \text{ A}$.

Sait

$$S_0 = \sqrt{3} \cdot V I_0 = \sqrt{3} \cdot 380 \cdot 74$$
$$S_0 = 48,705 \text{ VAR}$$

~~$$Q_0 = \sqrt{S_0^2 - P_0^2} = \sqrt{48,7^2 - 4,8^2}$$~~
$$Q_0 = 48,46 \text{ KVAR}$$


$$Q_0 = \frac{3V^2}{X_f} \quad X_f = \frac{3V^2}{Q_0}$$

$$X_f = \frac{3 \cdot 220^2}{48,46 \cdot 10^3} = 2,99 \Omega$$

$$X_f = 2,99 \Omega$$

- Essai en court circuit

$P_{R'_2 cc}$?

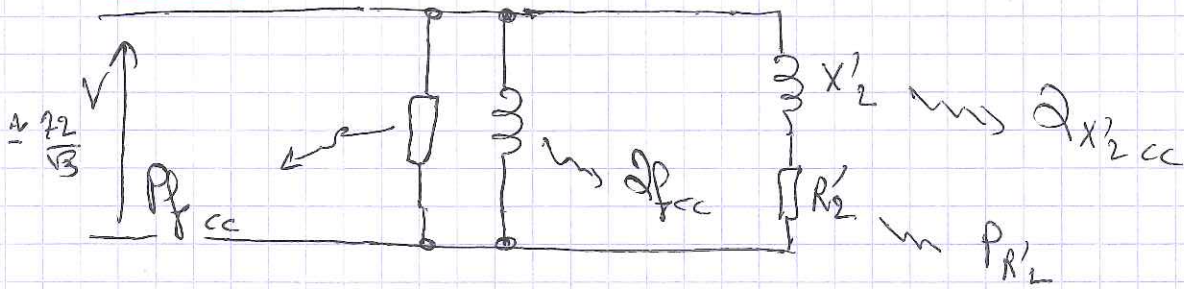

$$P_{cc} = 7400 \text{ W} = P_{R_1 cc} + P_{f cc} + P_{R'_2 cc}$$

$I_{cc} = 220 \text{ A}$, on considère que $P_{f cc} \approx \frac{3V_{cc}^2}{X_f}$

d'où $P_{cc} = 3R_1 I_{cc}^2 + \frac{3 \times V_{cc}^2}{X_f} + P_{R'_2 cc}$

Soit $P_{R'_2 cc} = P_{cc} - 3R_1 I_{cc}^2 - \frac{3V_{cc}^2}{X_f}$

$$= 7400 - 3 \times 20 \times 10^{-3} \times 220^2 - \frac{3 \times 72^2}{30,25 (\sqrt{3})^2}$$

$$P_{R'_2 cc} = 7400 - 2904 - 1713,7$$

$$P_{R'_2 cc} = 4324,6 \text{ W}$$

$Q_{X'_2 cc}$?

$$S_{cc} = \sqrt{3} \times V_{cc} \times I_{cc}$$

$$= \sqrt{3} \times 72 \times 220$$

$$S_{cc} = 27\,435,68 \text{ VA}$$

$$Q_{cc} = \sqrt{S_{cc}^2 - P_{cc}^2} = \sqrt{27,435^2 - 7400^2}$$

$$Q_{cc} = 26,418 \text{ kVAR}$$

$$Q_{X'_2} = Q_{cc} - Q_{f cc} = Q_{cc} - \frac{3V^2}{X_f}$$

$$Q_{X'_2} = 26,418 - \frac{3 \times 72^2}{2,99 \times (\sqrt{3})^2} = 26,418 - 1733,7$$

$$= 24\,684,2 \text{ VAR}$$

Exc 5 (suite)

Établissent les valeurs de R'_2 et X'_2

Avec $P_{R'_2 cc}$ et $Q_{X'_2 cc}$

On peut avoir

$$S_{2'2 cc} = \sqrt{P_{R'_2 cc}^2 + Q_{X'_2 cc}^2}$$

$$= \sqrt{4324,6^2 + 24684,2^2}$$

$$S_{2'2 cc} = 25060,18 \text{ VA.}$$

$$I_{bt} = \frac{S_{2'2 cc}}{\sqrt{3} U_{1 cc}} = \frac{25060,18}{\sqrt{3} \times 72}$$

$$I_{bt} = 200,95 \text{ A}$$

d'où


$$R'_2 = \frac{P_{R'_2 cc}}{3 I_{bt}^2}$$

$$R'_2 = \frac{4324,6}{3 \times 200,95^2} = 35,69 \text{ m}\Omega$$

$$X'_2 = \frac{Q_{X'_2 cc}}{3 I_{bt}^2} = \frac{24684,2}{3 \times 200,95^2}$$

$$X'_2 = 0,2037 \Omega$$

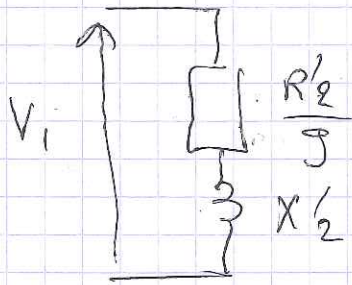→ Pour un glissement de $\cdot g = 2,6\%$.



Calcul de I_{1t} :

$$I_{1t} = \frac{V_1}{\sqrt{\left(\frac{R_2}{g}\right)^2 + X_2^2}} = \frac{220}{\sqrt{\left(\frac{35,69 \cdot 10^{-3}}{0,026}\right)^2 + 0,903^2}}$$

$$I_{1t} = \frac{220}{1,38} = 158,54 \text{ A}$$

donc $P_{TR} = 3 \frac{R_2}{g} \cdot I_{1t}^2 = 3 \times \frac{35,69 \cdot 10^{-3}}{0,026} \times 158,54^2$


$$P_{TR} = 3 \times 1,372 \cdot 158,54^2 = 103 \text{ 507 W}$$

$$T_{em} = \frac{P_{TR}}{\left(\frac{2\pi n_p}{60}\right)} = \frac{103 \text{ 507}}{\left(\frac{2\pi \times 1000}{60}\right)} = \frac{103 \text{ 507}}{104,71}$$

$$T_{em} = 988 \text{ Nm}$$

$I_1 = ?$
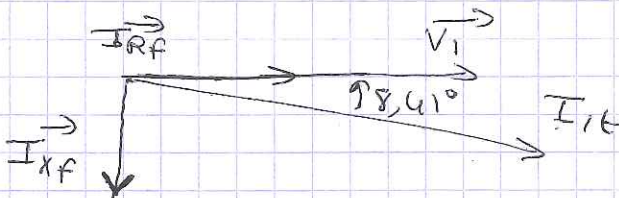
$$\varphi_{2/2} = \text{Atan} \frac{X_2}{\left(\frac{R_2}{g}\right)} = 8,61^\circ$$



$$I_{rf} = \frac{V_1}{R_f} = \frac{220}{30,25} = 7,27 \text{ A}$$

$$I_{xf} = \frac{V_1}{X_f} = \frac{220}{2,99} = 73,57 \text{ A}$$

$$I_1 = \sqrt{\left(I_{1t} \cos 8,61 + I_{rf}\right)^2 + \left(I_{xf} + I_{1t} \sin 8,41\right)^2}$$

$$= \sqrt{\left(158,54 \cos 8,41 + 7,27\right)^2 + \left(73,57 + 158,54 \sin 8,41\right)^2}$$


$$= \sqrt{164,1^2 + 96,75^2} = 190,5 \text{ A}$$

$\cos \varphi = ?$

$$\cos \varphi = \cos \text{Atan} \left(\frac{96,75}{164,1}\right) = \cos(30,52) = 0,86$$

Ex 5 (Suite)

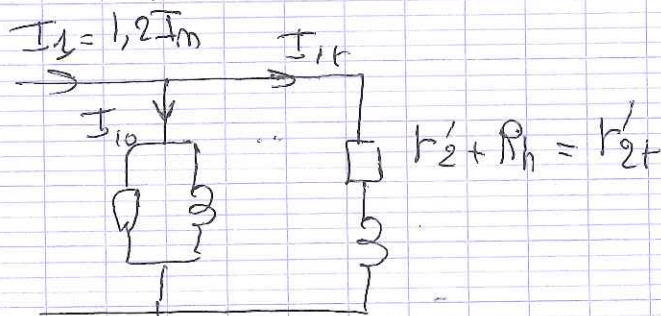3) On place des résistances au rotor pour le démarrage.



On prend $I_r = 200 \text{ A}$


Soit $I_d = 1,2 \times 200 = 240 \text{ A}$

Détermination de I_d .



(H) On néglige I_{rf} devant I_{xf}

On obtient

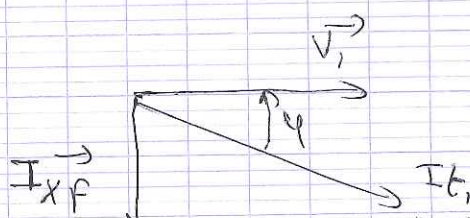


$$I_d = \sqrt{(I_{xf} + I_{r_2} \sin \varphi)^2 + (I_r \cos \varphi)^2}$$

$$I_d^2 = (I_{xf} + I_r \sin \varphi)^2 + (I_r \cos \varphi)^2$$

On va calculer I_d au démarrage en négligeant R_f devant X_f .

Don p'approximation:

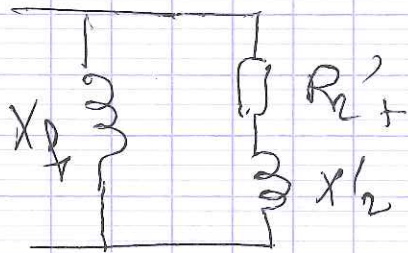

$$\underline{Z} = \frac{1}{\frac{1}{jX_f} + \frac{1}{R'_2t + jX'_2}}$$

$$\underline{Z} = \frac{R'_2t + j(X'_2 + X_f)}{j(X_f)(R'_2t + jX'_2)}$$

$$\underline{Z} = \frac{R'_2t + j(X'_2 + X_f)}{-X_f X'_2 + j R'_2t \cdot X_f}$$

$$|\underline{Z}| = \sqrt{\frac{R'^2_{2t} + (X'_2 + X_f)^2}{(X_f X'_2)^2 + (R'_2t \cdot X_f)^2}}$$

Don donnée $|\underline{I}_L| = 1,2 \text{ A} = \frac{(V_L)}{|\underline{Z}|}$

$$\underline{Z} = \frac{220}{240} = 0,916 \Omega$$

Don constant $X_f = 9,992 \quad X'_2 = 0,203$

Don $|\underline{Z}|^2 = 0,916^2 = 0,840 \Omega^2$

ex 5 (Suite)

ex 3.

$$z^2 \left[(X_{\phi} X'_{\phi})^2 + (R'_{2t} X_{\phi})^2 \right] = R'_{2t}{}^2 + (X'_{\phi} + X_{\phi})^2$$

$$z^2 \cdot (X_{\phi} X'_{\phi})^2 + z^2 \cdot R'_{2t}{}^2 \cdot X_{\phi}^2 = R'_{2t}{}^2 + (X'_{\phi} + X_{\phi})^2$$

$$R'_{2t}{}^2 \left[1 - (z \cdot X_{\phi})^2 \right] = (z \cdot X_{\phi} X'_{\phi})^2 - (X'_{\phi} + X_{\phi})^2$$

$$R'_{2t}{}^2 = \frac{(z \cdot X_{\phi} X'_{\phi})^2 - (X'_{\phi} + X_{\phi})^2}{1 - (z \cdot X_{\phi})^2}$$

$$R'_{2t} = \sqrt{\quad}$$

$$R'_{2t} = \sqrt{\frac{(0,916 \times 2,99 \cdot 0,203)^2 - (0,203 + 2,99)^2}{1 - (0,916 \cdot 2,99)^2}}$$

$$R'_{2t} = \sqrt{\frac{0,555^2 - 10,195}{1 - 7,50}}$$

$$R'_{2t} = \sqrt{\frac{0,589}{6,50}} = \sqrt{1,52}$$

$$R'_{2t} = 1,233 \Omega$$

Donc le réostat sera

$$R_h + R'_{\phi} = 1,233 \Omega$$

$$R_h = 1,233 - 0,0356$$


$$R_h = 1,198 \Omega$$

$$\Rightarrow \text{au démarrage : } P_{TR} = 3 R'_{\phi} \cdot I_{it}^2 = 3 \times 1,233 \times \frac{V}{\sqrt{1,233^2 + 0,203^2}}$$

$$T_{\text{démarrage}} = \frac{P_{TR}}{\omega} = \frac{114580}{104,71} = 1100 \text{ Nm}$$

Calcul de la puissance transmise à
 $g = 2,6\%$.

Soit.

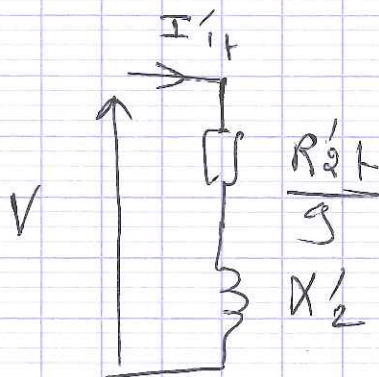

$$I'_{1t} = \frac{V}{\sqrt{\left(\frac{R'_{2t}}{g}\right)^2 + (X'_2)^2}} = \frac{220}{\sqrt{\left(\frac{1,933}{0,026}\right)^2 + (0,93)^2}}$$

$$I'_{1t} = \frac{220}{47,42} = 4,63 \text{ A.}$$

$$P_{tr} = 3 \frac{R'_{2t}}{g} \times I_{1t}^2 = 3 \times 47,42 \times 4,63^2$$

$$P_{tr} = 3049,81 \text{ W}$$

$$T_{dispo} = \frac{P_{tr}}{\left(\frac{2\pi \cdot 1000}{60}\right)} = \frac{3049,81}{104,71}$$

$$T_{dispo} = 29,12 \text{ N.}$$

A cause des résistances au rotor, le couple dispo est lui-même réduit, il faut les éliminer au fur et à mesure de manière à retrouver le fort couple possible délivré par cette machine.