


3. le hachem 2 quadrants réversible
en courant:

(Suite).

B. (Suite)

entre 0 et αT .

D_1 passant, T_2 bloqué.

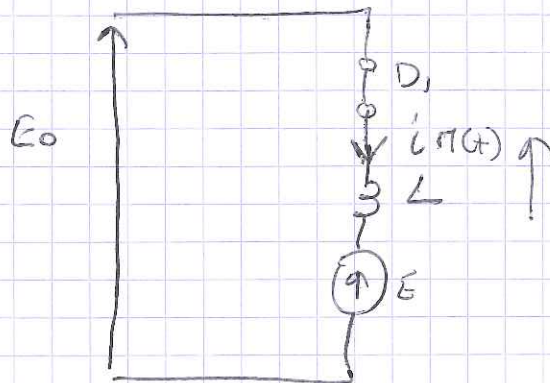


$$E_0 - L \frac{di}{dt} - E = 0$$

$$\frac{di}{dt} = \frac{E_0 - E}{L}$$

$$i_H(t) = \frac{E_0 - E}{L} t + k$$

$$\text{à } t=0 \quad i_H(0) = I_{\text{mini}}$$
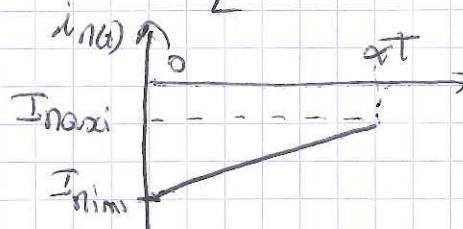
$$\text{Soit } i_H(t) = \frac{E_0 - E}{L} t + I_{\text{mini}}$$




3.2. forme d'ondes

Exercício 9:

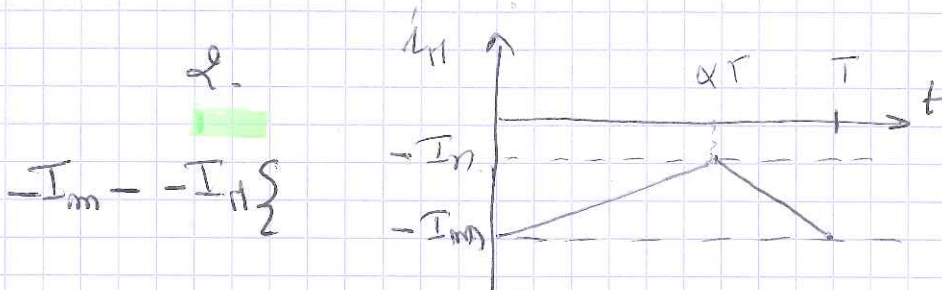1. $\langle u_{rr} \rangle = \frac{1}{T} (E_0 \cdot \alpha \cdot T)$

$\langle u_{rr} \rangle = E_0 \cdot \alpha$




$\langle i_{rr} \rangle = \frac{1}{T} \left(-I_{rr} \cdot \alpha T + \frac{(-I_m - -I_m)}{2} \cdot T \right)$


$= \frac{1}{T} \left(-I_{rr} \cdot T + \frac{I_{rr} - I_m}{2} \cdot T \right)$

$\langle i_{rr} \rangle = -\frac{(I_{rr} + I_m)}{2}$

3.

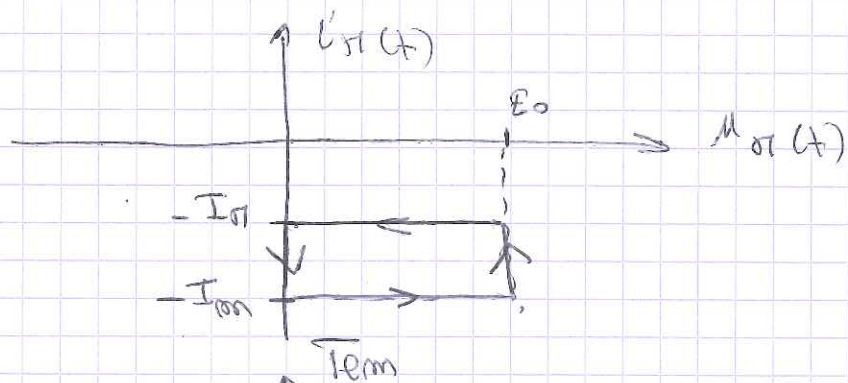

4.

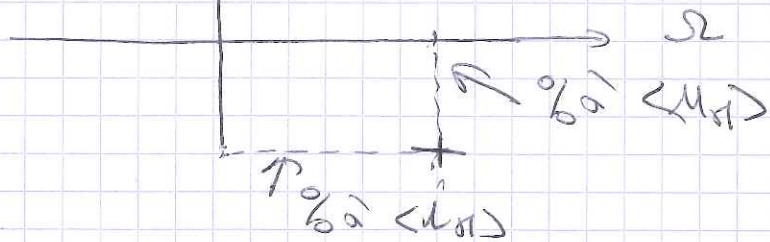

Exercice 10:

1. D est bloqué quand
H est passant con

$$V_H = -E_c$$


2.

$$i_s(E)$$


$$E - L \frac{di}{dt} = 0$$

$$i = \frac{E}{L} \cdot t + k$$

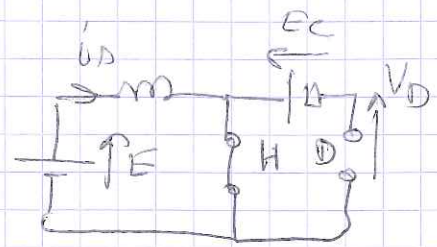
à $t=0$ $i(0) = I_{m}$ et $i(t) = \frac{E}{L} \cdot t + I_{m}$



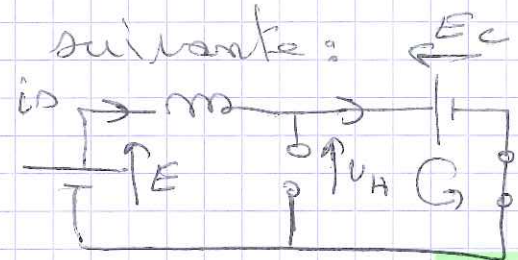3. Quand H est ouvert.
le courant i_s circule dans la
maille suivante:




$$V_H - E_c = 0 \Rightarrow V_H = E_c$$

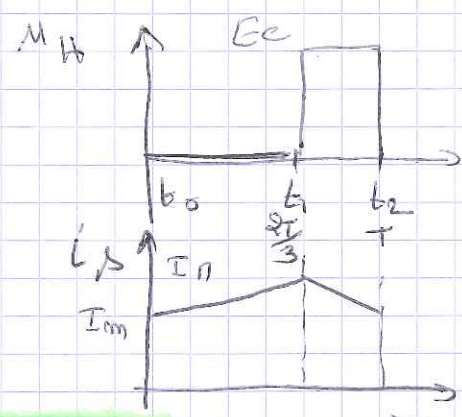

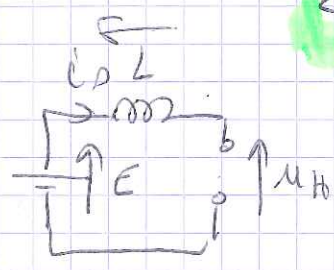4.

$$\langle V_H \rangle = \frac{1}{T} E_c \cdot \frac{2}{3} = \frac{E_c}{3}$$



$$E - L \frac{di}{dt} - V_H = 0$$

$$\langle V_H \rangle = E \Rightarrow \text{donc } \frac{E_c}{3} = E$$

$$E_c = 3E$$

$(E_c = 144V)$

5.

$$\Delta I_s = I_{rt} - I_m$$

On sait que

$$i_s(t) = \frac{E}{L} t + I_m$$

$$i_s\left(\frac{2T}{3}\right) = I_{rt} = \frac{E}{L} \cdot \frac{2T}{3} + I_m$$

$$\Delta I = \frac{E}{L} \cdot \frac{2}{3} T$$

$$\Delta I = \frac{48}{25 \cdot 10^{-3}} \times \frac{2}{3} \times 0,5 \cdot 10^{-3}$$

$$\Delta I = 0,64 \text{ A}$$


$$I_{s\text{max}} = \Delta I + I_{s\text{min}} = 0,64 + 12$$

$$I_{s\text{max}} = 12,64 \text{ A}$$

5. bachem leue quadrants reversible en l'emission.

Exercice 66:

entre 0 et αT :

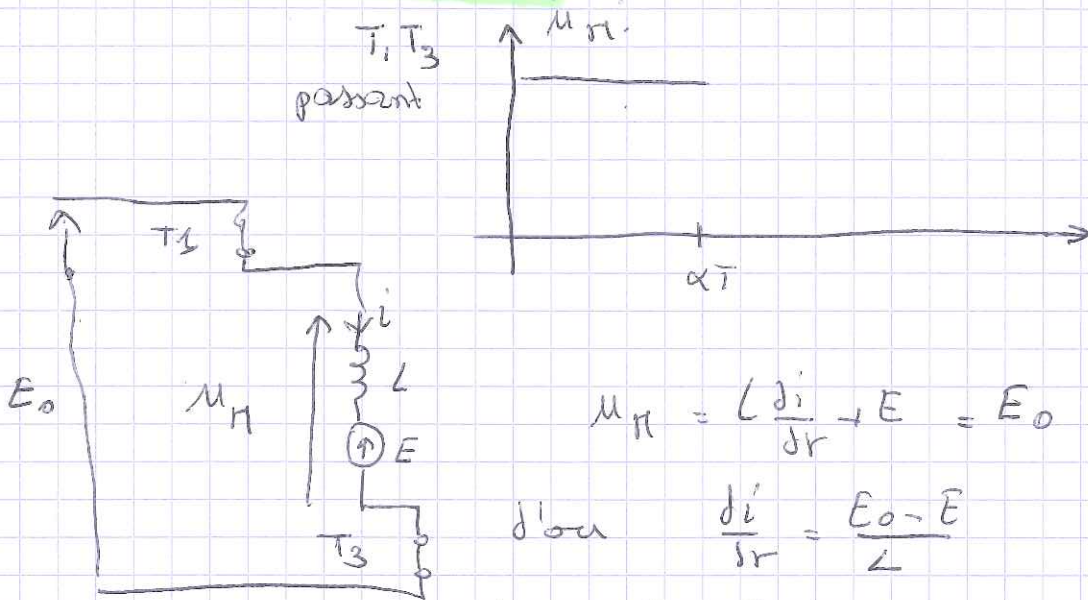


$$\phi_M = L \frac{di}{dt} + E = E_0$$

d'où $\frac{di}{dt} = \frac{E_0 - E}{L}$


$$i(t) = \frac{E_0 - E}{L} t + k$$

à $t=0 \Rightarrow i(0) = I_{com}$. d'où $k = I_{com}$.

$$i(t) = \frac{E_0 - E}{L} t + I_{com}$$

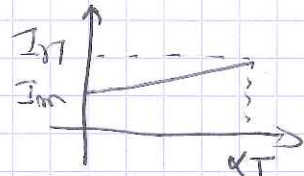

entre T et αT :

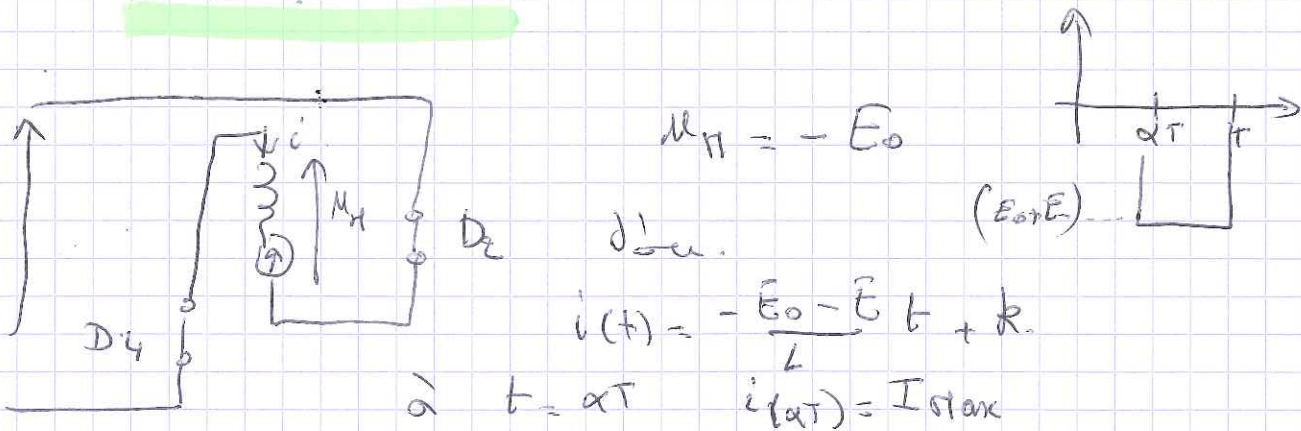

$$\phi_M = -E_0$$

d'où.


$$i(t) = -\frac{E_0 + E}{L} t + k$$

à $t = \alpha T$ $i(\alpha T) = I_{max}$

$$I_{max} = -\frac{(E_0 + E)}{L} \alpha T + k \Rightarrow k = I_{max} + \frac{(E_0 + E)}{L} \alpha T$$

Soit $i(t) = -\frac{(E_0 + E)}{L} t + I_{max} + \frac{(E_0 + E)}{L} \alpha T$
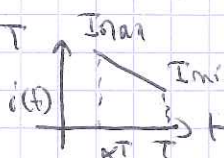
$$i(t) = -\frac{(E_0 + E)}{L} (t - \alpha T) + I_{max}$$



Forme d'ondes: → Voir doc. cours.


$$\begin{aligned} 5 \quad \langle u_{\pi} \rangle &= \frac{1}{T} \left((E_0 - E) \alpha T - (E_0 + E) (T - \alpha T) \right) \\ &= \frac{1}{T} \left((E_0 - E) \alpha - (E_0 + E) (1 - \alpha) \right) \\ &= \left(\underline{E_0 \alpha} - \underline{E \alpha} - E_0 - E + \underline{E_0 \alpha} + \underline{E \alpha} \right) \\ &= \left(2 E_0 \alpha - (E_0 + E) \right) \\ \langle u_{\pi} \rangle &= 2 \alpha \cdot E_0 - (E_0 + E) \\ &= E_0 (2\alpha - 1) - E \end{aligned}$$

6

Si $\alpha = 0$ $\langle u_{\pi} \rangle = - (E_0 + E)$

Si $\alpha = 1$
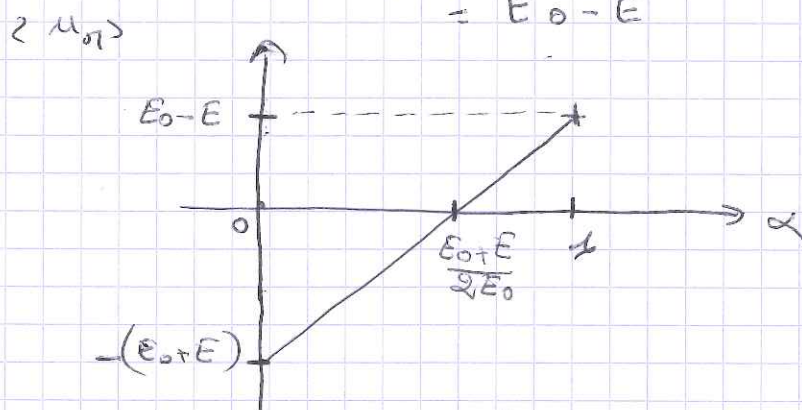
$$\langle u_{\pi} \rangle = 2 E_0 - E_0 - E = E_0 - E$$



Pour la valeur nulle de $\langle u_{\pi} \rangle$:


$$0 = E_0 (2\alpha_1 - 1) - E$$

$$2\alpha_1 - 1 = \frac{E}{E_0}$$

$$2\alpha_1 = 1 + \frac{E}{E_0}$$

$$\alpha_1 = \frac{1}{2} \left(1 + \frac{E}{E_0} \right) = \frac{E_0 + E}{2E_0}$$

7. Pt de jonction

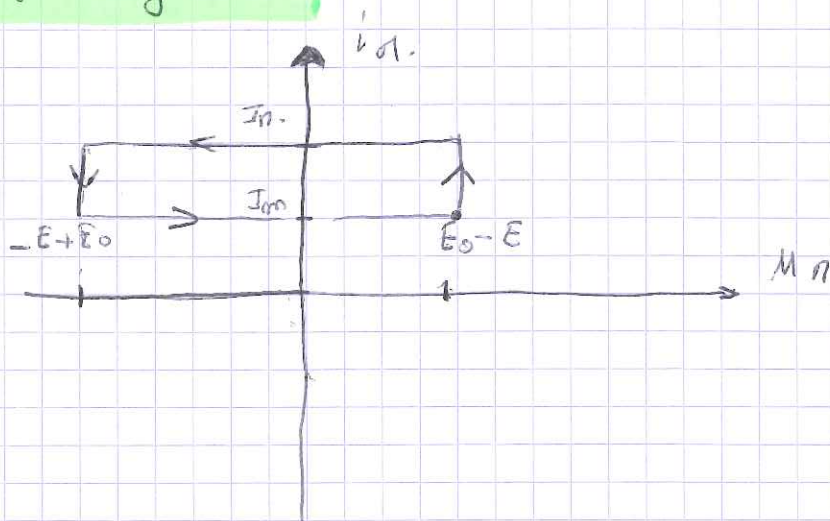

8. Grandeur mécanique

$$\text{Si } \alpha < \frac{E_0 + E}{2E_0}$$

$$\langle M_n \rangle < 0$$

